

# Digital systems


## Practicum 12



By: Naura salsabila  
NIM = L200183159

Informatics Engineering  
Faculty of Information and Communication  
University of Muhammadiyah Surakarta


## Experiment 1

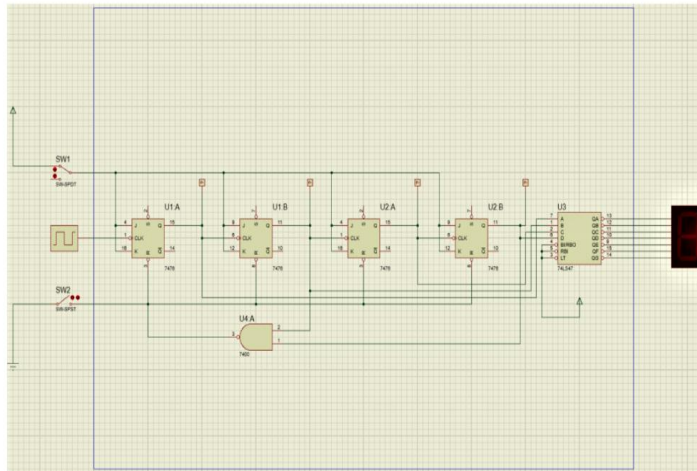

1. What is the output seen in the seven segment?

Answer: The seven segment output is in the form of calculations from 1 to 9.

## Experiment 2

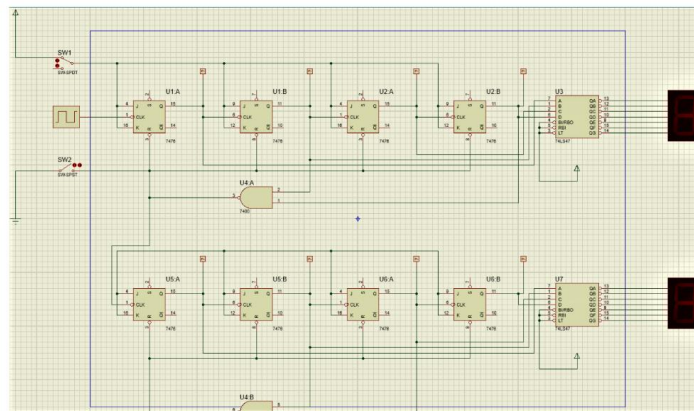

1. What is the clock function in the series above?

Answer: To determine the speed of calculation.

2. Explain the usefulness of the SPDT Switch in the series above!

Answer: To check the value of the decoder.

3. Explain the usefulness of the SPST Switch in the series above!

Answer: To stop counting.

### Additional Assignment

